

ICE-3103, Microwave Engineering (Smith Chart)



Tanvir Zaman Khan

Assistant professor

Dept. of Information & Communication Engineering

Noakhali Science and Technology University

Noakhali-3814, Bangladesh


We have to find out using Smith chart

- a) Voltage reflection coefficient, Γ
- b) Voltage standing-wave ratio, **VSWR**
- c) Finding input impedance, Z_{in}
- d) Finding load impedance, Z_L
- e) the distances of the voltage maximum and voltage minimum, d_{max} , d_{min} **OR** l_{max} , l_{min}

Set: A1 Question

A $50\text{-}\Omega$ lossless line is terminated in a load impedance, $Z_L = (25+j50)\Omega$. Use the smith chart to find

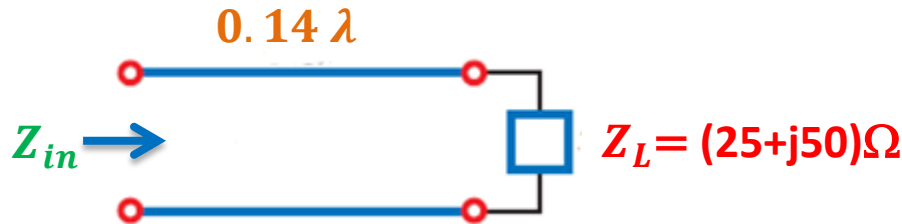- a) voltage reflection coefficient,
- b) the voltage standing-wave ratio,
- c) the input impedance of the line, given the line is 0.14λ



Solution:

Normalized load impedance, $Z_L = \frac{25\ \Omega}{50\ \Omega} + j \frac{50\ \Omega}{50\ \Omega} = 0.5 + j1$

Ans: Normalized, $Z_L = 0.5 + j1$

a) $\Gamma = 0.62 \angle 83^\circ$

b) $VSWR = 4.2$

c) Normalized $Z_{in} = 0.3 - j1.8$;

Point B= reflection coefficient angle


Point C= wavelength

Point A= load impedance

Point D= VSWR

Point D= VSWR
VSWR=4.2

Point B= Angle
= $\angle 83^\circ$

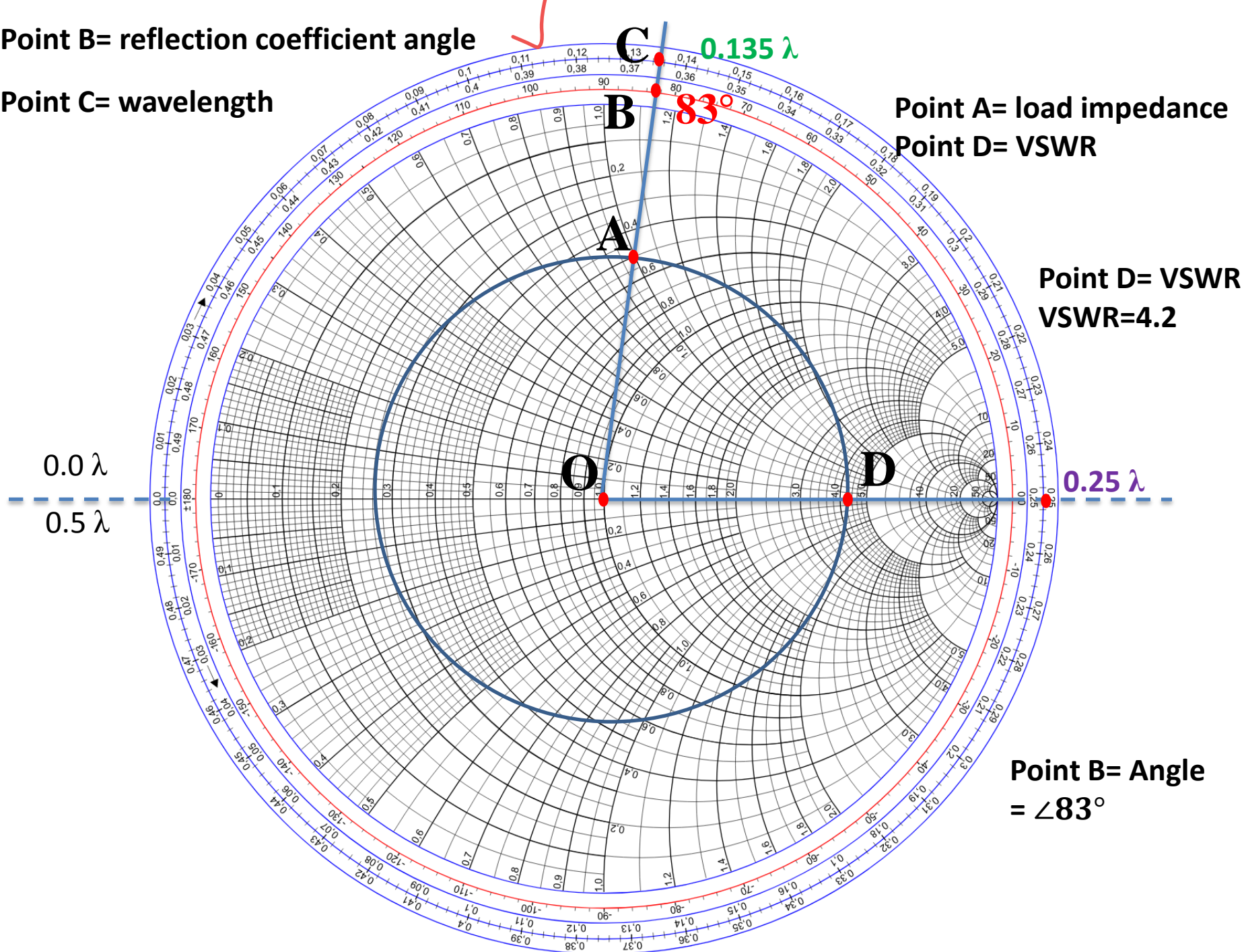


$$\text{VSWR} = 4.2$$

$$\text{Voltage reflection coefficient, } \Gamma = 0.62 \angle 83^\circ$$

Magnitude


Angle

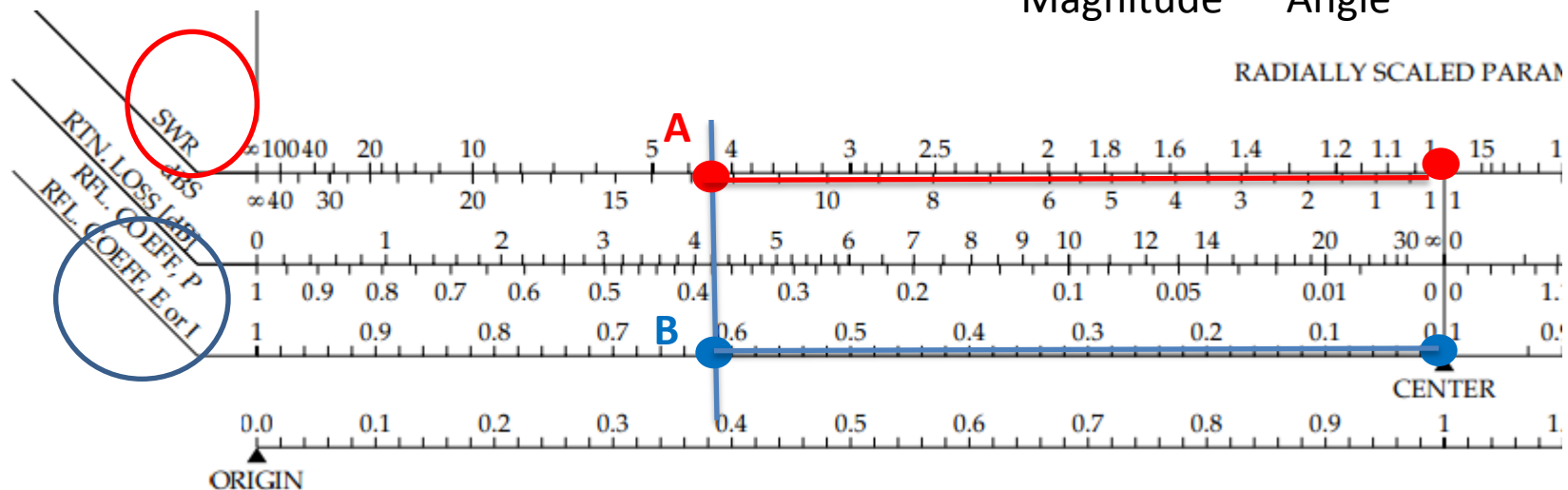

Input impedance Towards 0.14λ

$(0.135+0.14)= 0.275 \lambda$

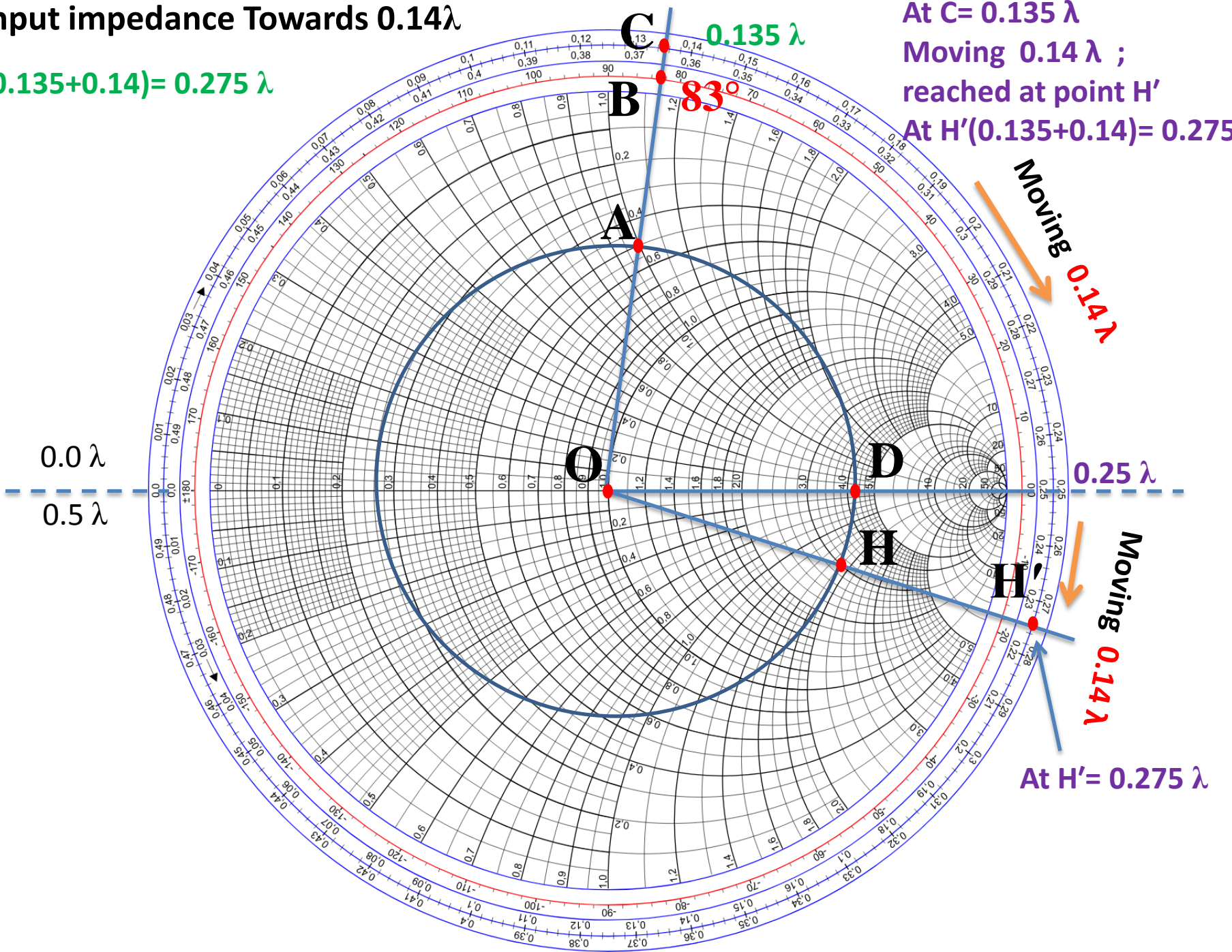
At C= 0.135λ
Moving 0.14λ ;
reached at point H'
At H'($0.135+0.14$)= 0.275λ



Input impedance Towards 0.14λ

$(0.135+0.14)= 0.275 \lambda$

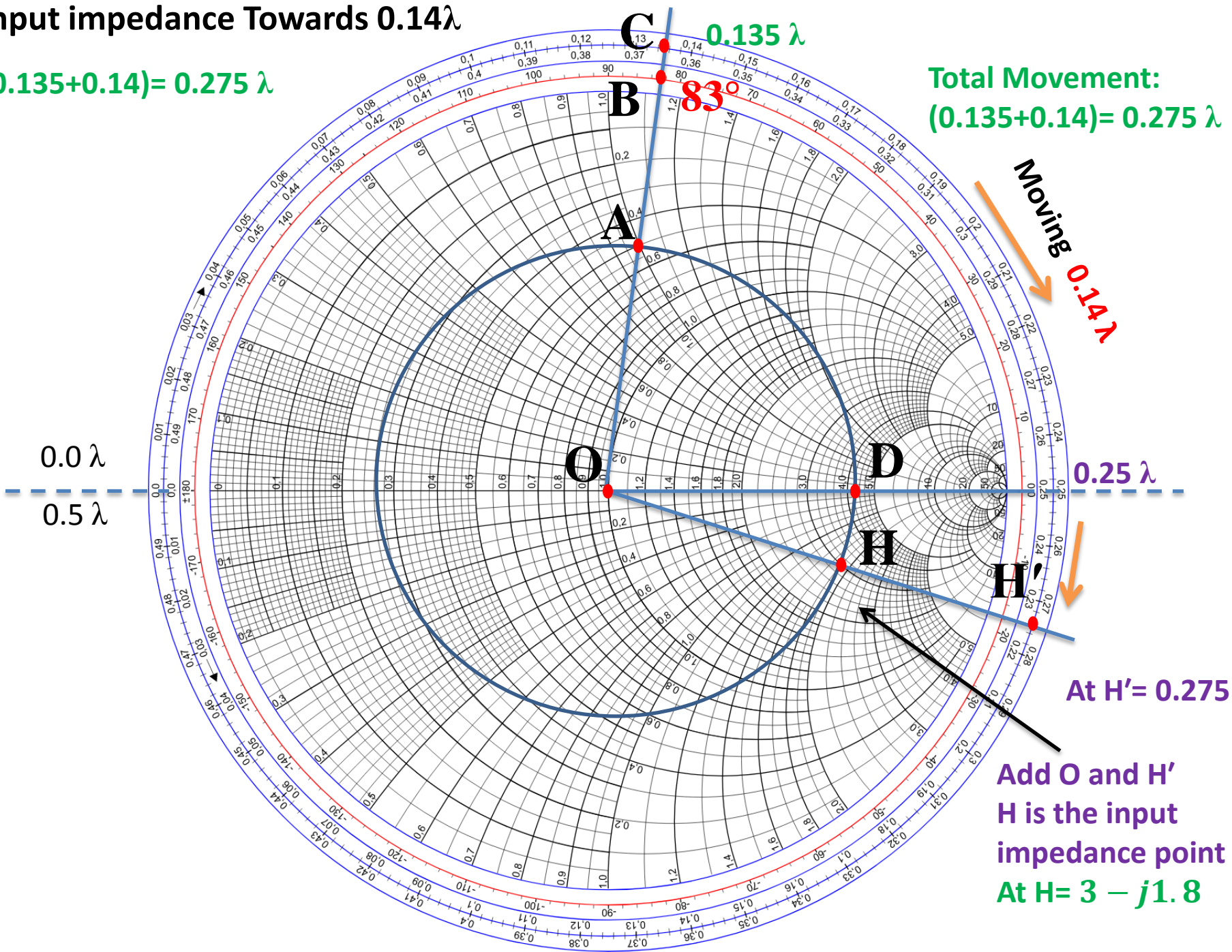Total Movement:
 $(0.135+0.14)= 0.275 \lambda$



At $H' = 0.275 \lambda$

Add O and H'
H is the input
impedance point
At $H = 3 - j1.8$

S is numerically equal to the value of r_0 at P_{\max} , the point at which the SWR circle intersects the real Γ axis to the right of the chart's center.

$$S = 4.2$$

$$\text{At } H = 3 - j1.8$$



R



X

So the input impedance, $\underline{Z_{in}}$ at H = $\frac{(3-j1.8) Z_0 \Omega}{}$


$$\begin{aligned} &= (3-j1.8) 50 \Omega \\ &= (150 - j90) \Omega \end{aligned}$$

Set: A2 Question

A $50\text{-}\Omega$ lossless line is terminated in a load impedance,

$Z_L = (25 + j50)\Omega$. Use the smith chart to find

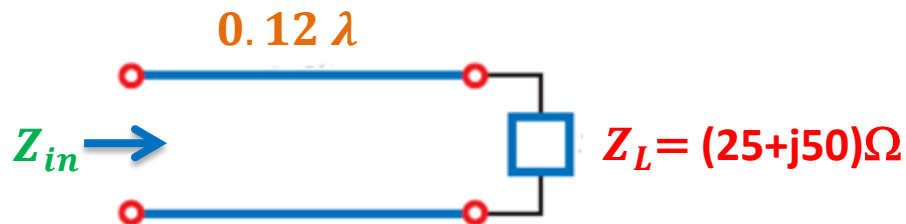
- a) voltage reflection coefficient,
- b) the voltage standing-wave ratio,
- c) the input impedance of the line, given the line is 0.12λ




Solution:

Normalized load impedance, $Z_L = \frac{25\ \Omega}{50\ \Omega} + j \frac{50\ \Omega}{50\ \Omega} = 0.5 + j1$

Input impedance Towards 0.12λ

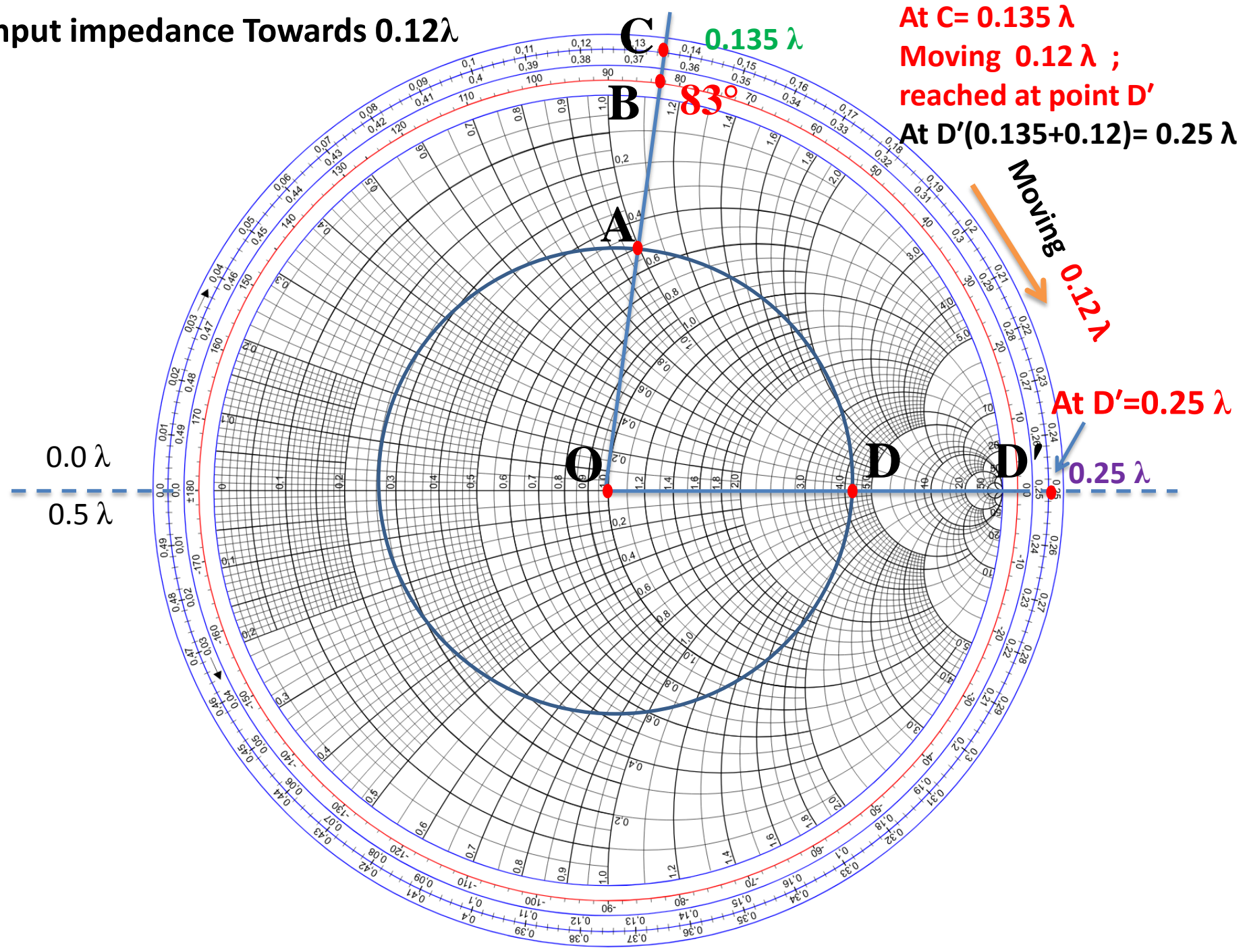

Input impedance Towards 0.12λ

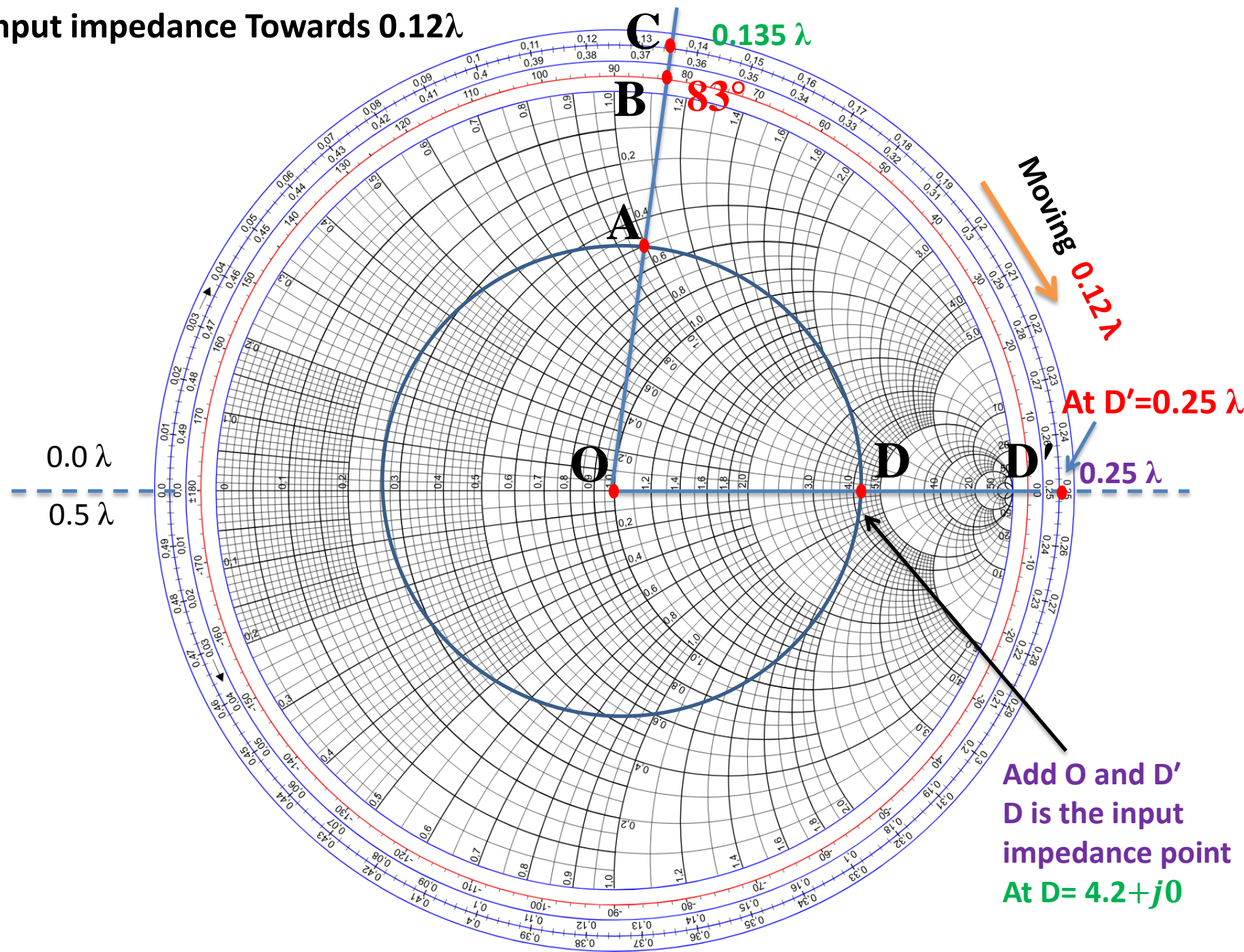

Add O and D'
D is the input
impedance point
At D= $4.2 + j0$

S is numerically equal to the value of r_0 at P_{\max} , the point at which the SWR circle intersects the real Γ axis to the right of the chart's center.

$$S = 4.2$$

$$\text{At } D = 4.2 + j0$$



R



X

$$\begin{aligned} \text{So the input impedance, } Z_{in} \text{ at } D &= (4.2 + j0)Z_0 \Omega \\ &= (4.2 + j0)50 \Omega \\ &= 210 \Omega \end{aligned}$$

Input impedance Towards 0.29λ

$(0.135+0.29)= 0.42 \lambda$

Point D'=After Moving 0.12λ


Point H'= After Moving 0.14λ

Point I'= After Moving 0.29λ
 $(0.135+0.29)= 0.42 \lambda$

At I'=0.42 λ


Moving 0.29λ

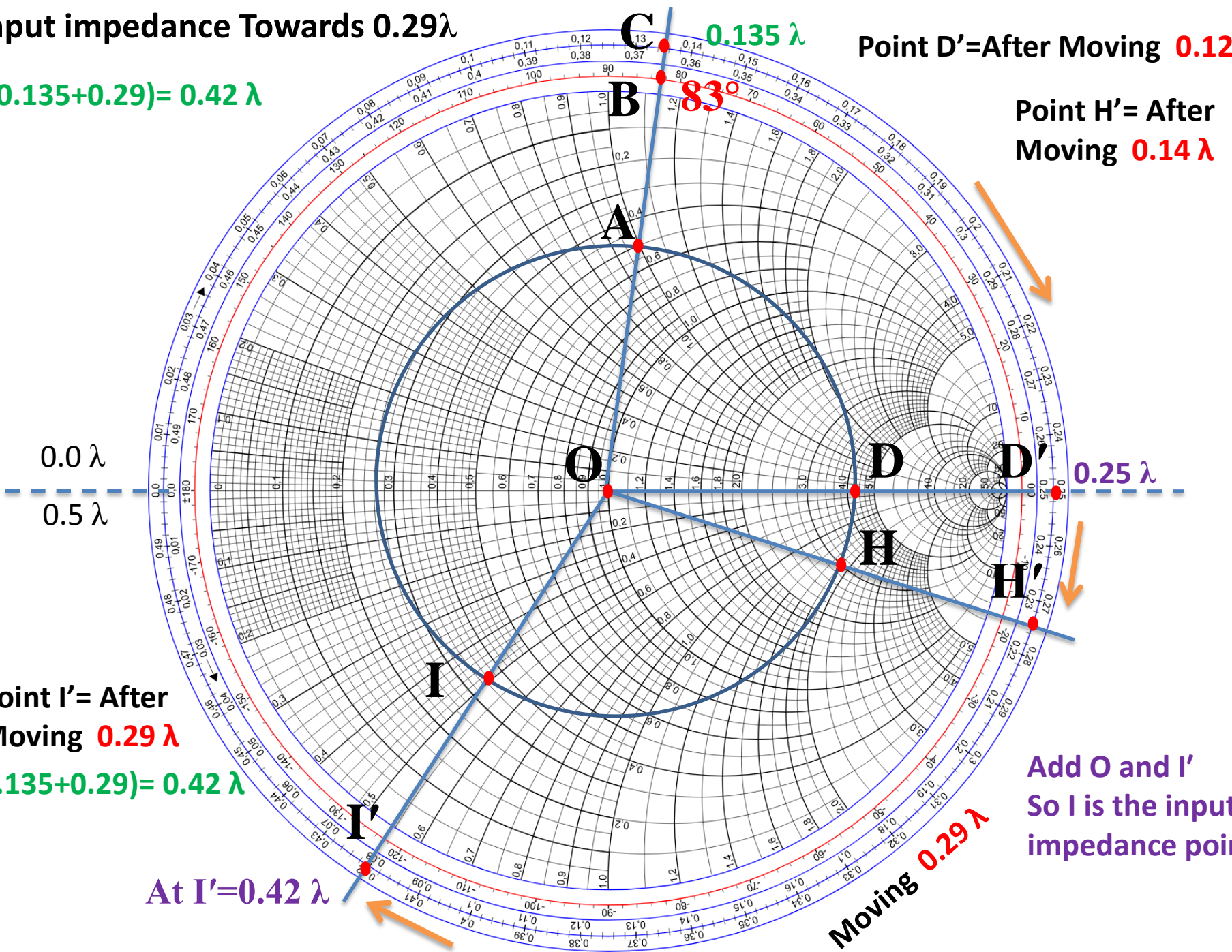Add O and I'
So I is the input impedance point



Input impedance Towards 0.6λ

Moving 0.6λ

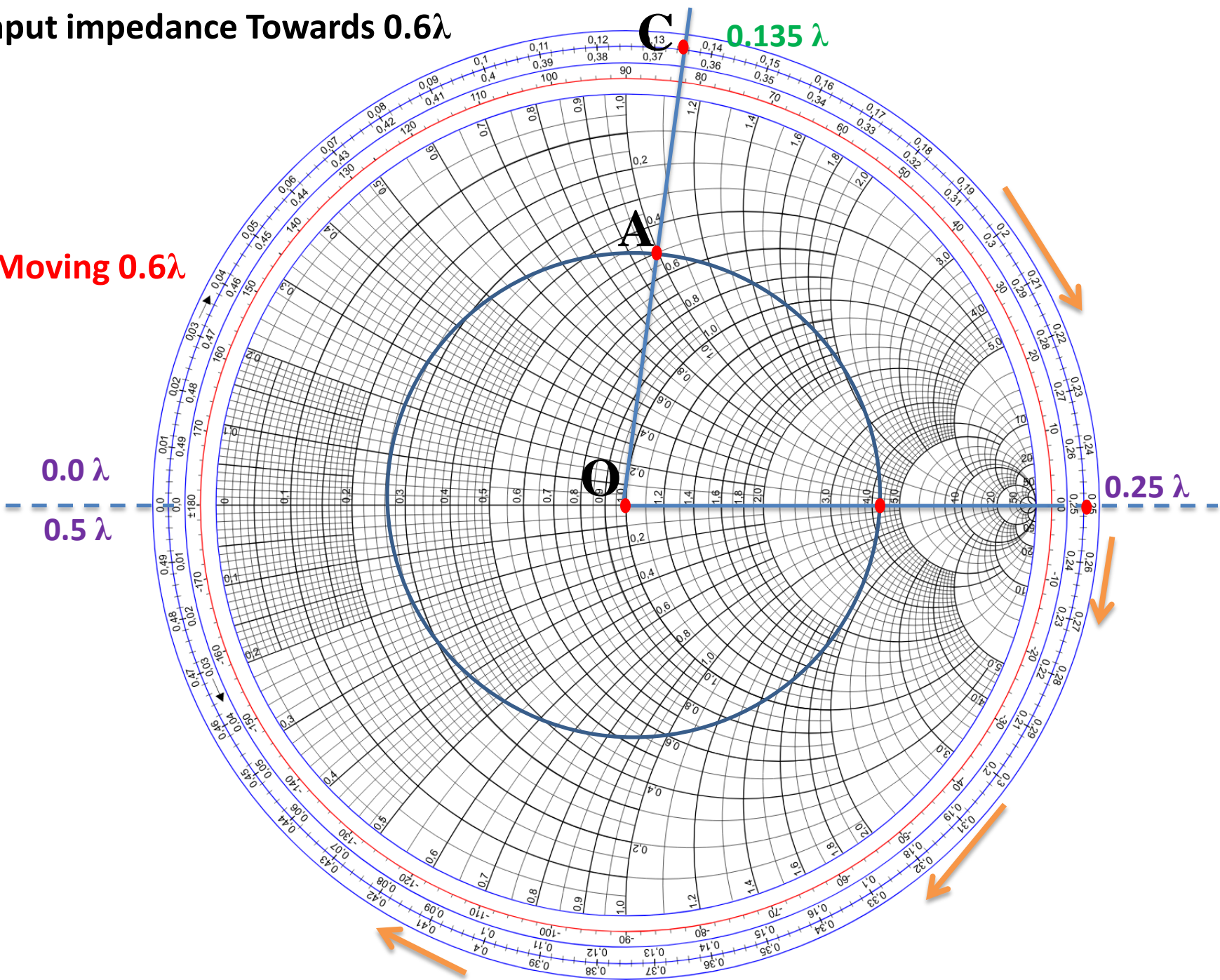

Input impedance Towards 0.6λ

Total Movement:
 $(0.135+0.6)= 0.735 \lambda$

K' is the resultant point

K'

K' = 0.23λ

 0.25λ

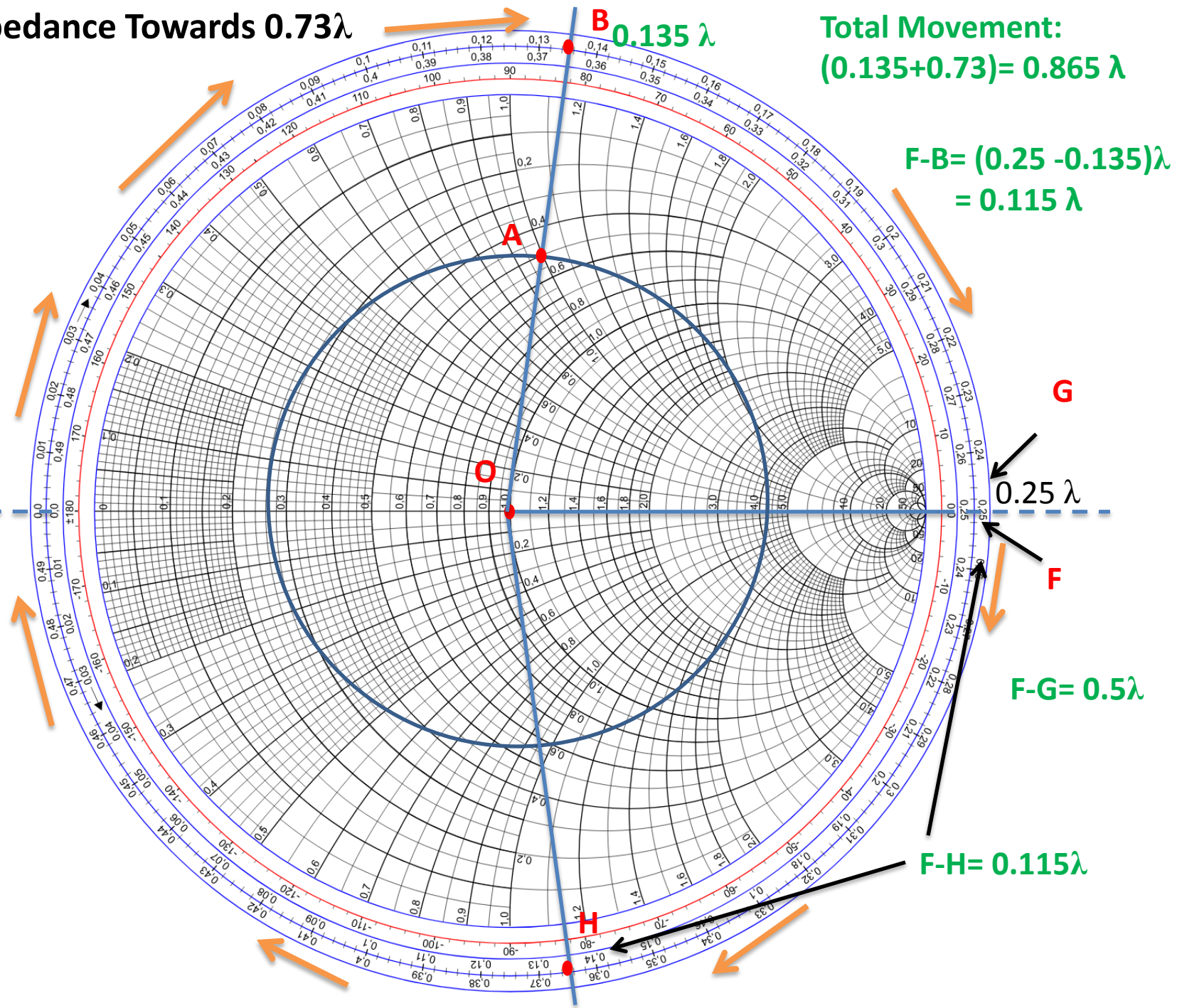
Add O and K'
So K is the input
impedance point

Moving 0.6λ

0.0 λ

0.5 λ

At Point G= $(0.135+0.12+0.25)= 0.5 \lambda$


$$(0.115+0.5+0.115+0.115)=0.73\lambda$$


Set: B Question

A $50\text{-}\Omega$ lossless line is terminated in a load impedance,

$Z_L = (50 + j100)\Omega$. Use the smith chart to find

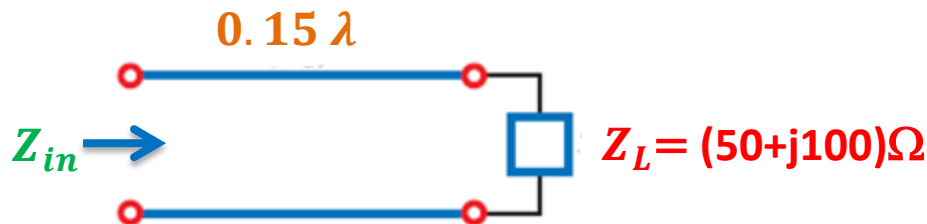- a) voltage reflection coefficient,
- b) the voltage standing-wave ratio,
- c) the input impedance of the line, given the line is 0.15λ




Normalized load impedance, $Z_L = \frac{50\ \Omega}{50\ \Omega} + j \frac{100\ \Omega}{50\ \Omega} = 1 + j2$

Set: C Question

A lossless transmission line is terminated in a normalized load impedance, $Z_L = (2-j1)\Omega$. Use the smith chart to find

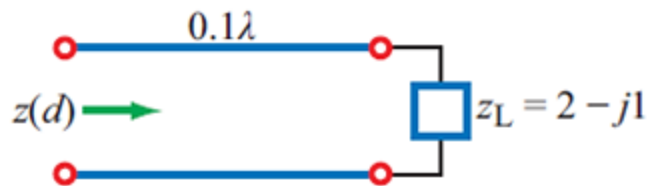
- a) voltage reflection coefficient,
- b) the voltage standing-wave ratio,
- c) the input impedance of the line, given the line is 0.1λ



Set: C Question

A lossless transmission line is terminated in a normalized load impedance, $Z_L = (2-j1)\Omega$. Use the smith chart to find

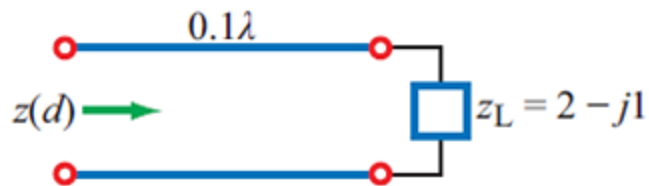
- a) voltage reflection coefficient,
- b) the voltage standing-wave ratio,
- c) the input impedance of the line, given the line is 0.1λ




Ans:

- a) voltage reflection coefficient= $0.45\angle -26.6^\circ$
- b) the voltage standing-wave ratio= 2.65
- c) the input impedance of the line, given the line is 0.1λ , = $0.6 - j0.66$

Set: C Question Solution

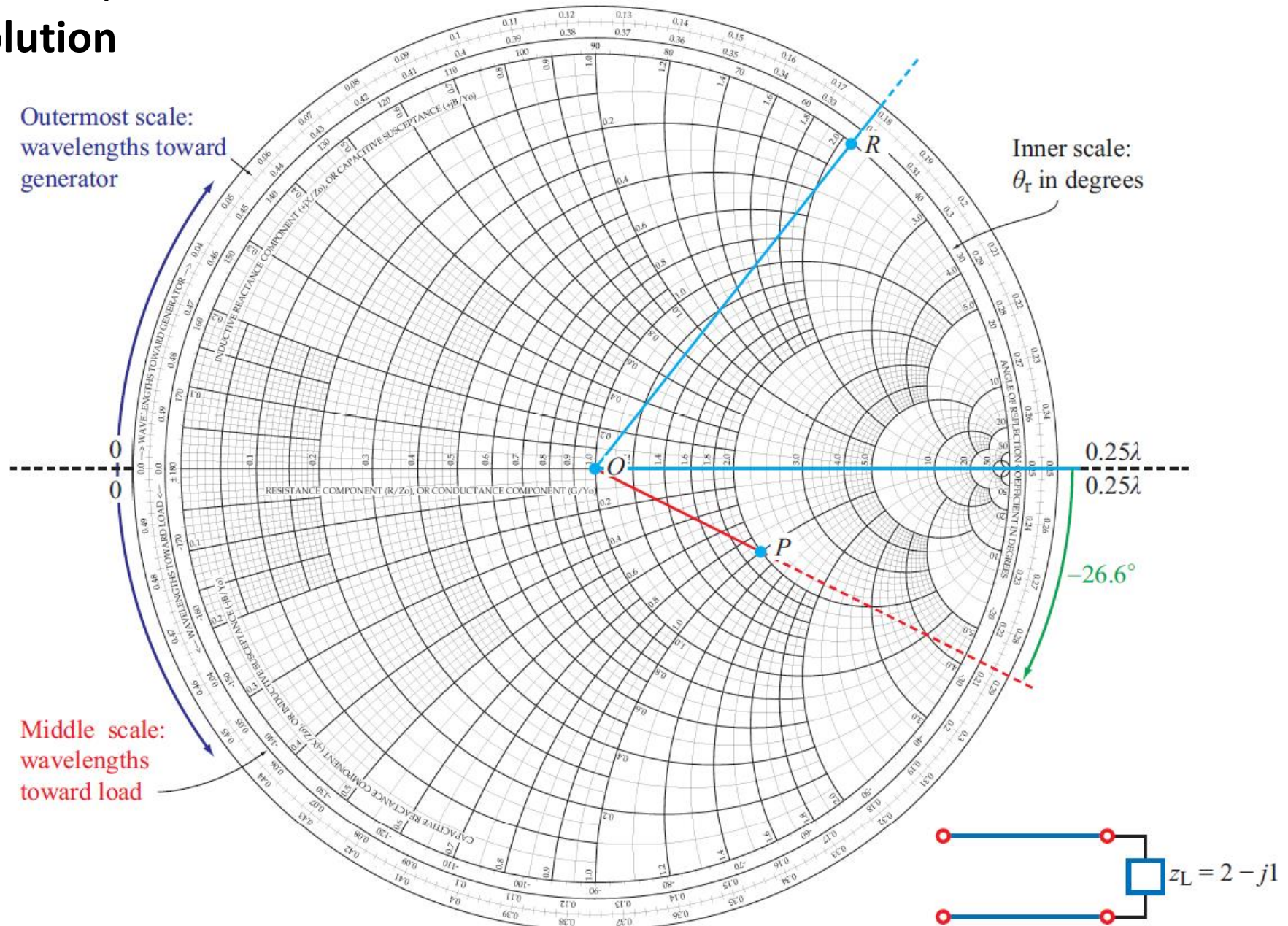


Set: C Question Solution

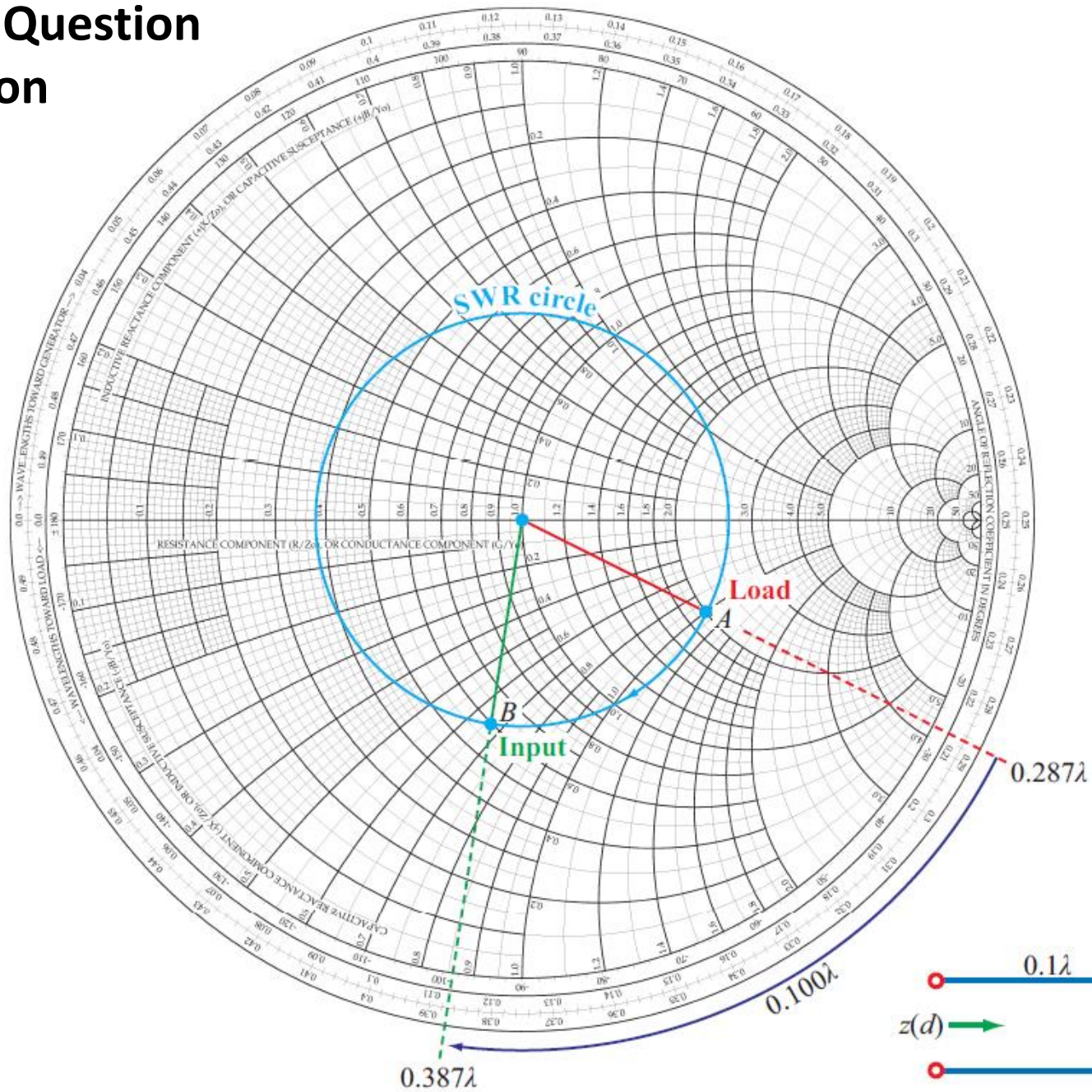


Finding Load Impedance, Z_L

Set: D Question

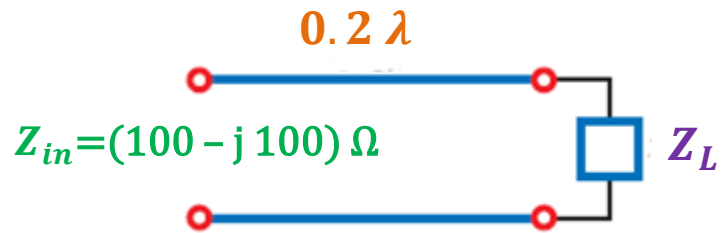

Finding Load Impedance, Z_L

Set: D Question

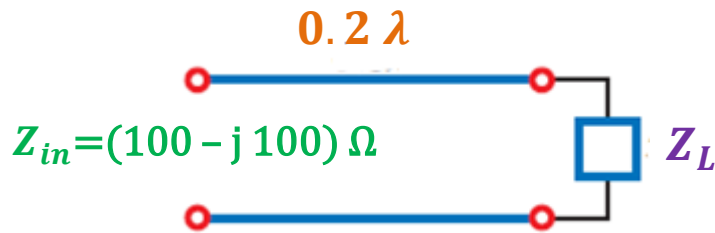

Solution:

Given:


$$Z_{in} = (100 - j100) \Omega$$

$$\begin{aligned} \text{So, Normalized input impedance, } Z_{in} &= \frac{100 \Omega}{50 \Omega} - j \frac{100 \Omega}{50 \Omega} \\ &= 2 - j2 \end{aligned}$$

$$\text{Ans: } Z_L = (0.35 + j0.55) Z_0 \Omega$$


Set: D Question Solution

Point A
= (0.35 + j 0.55)

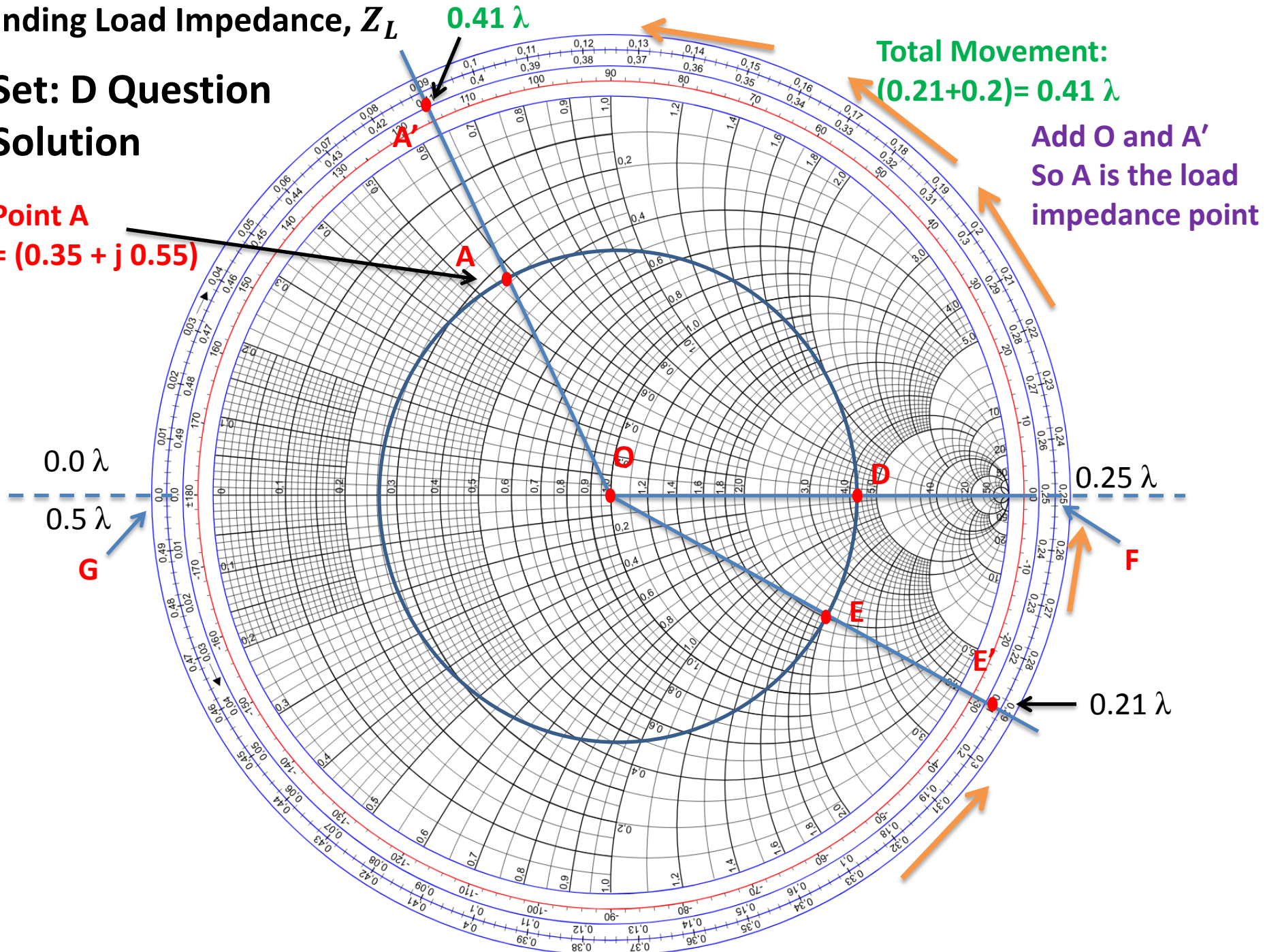

Maxima and Minima


$$VSWR = \frac{V_{max}}{V_{min}}$$

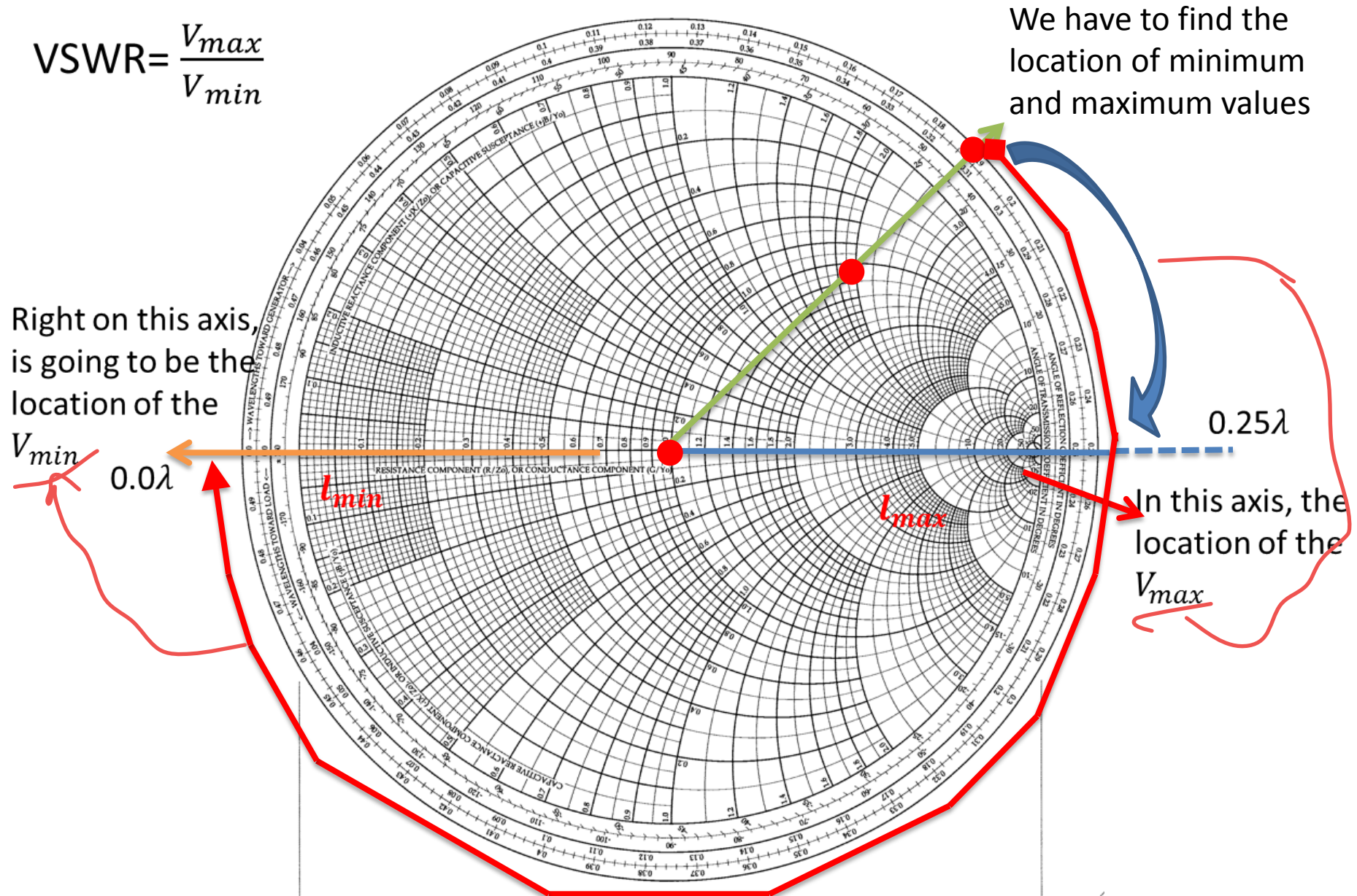

Maxima and Minima

Practice:

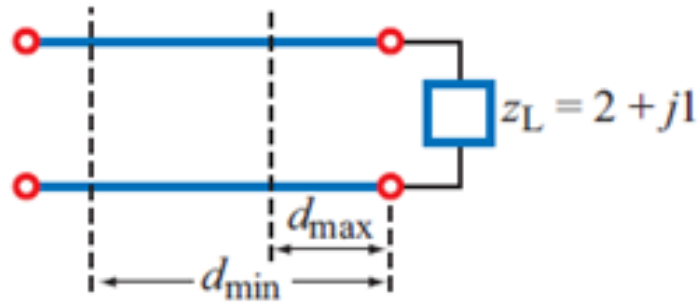Use the smith chart to find the distances of the first voltage maximum and first voltage minimum from the load



Ans:

first voltage maximum = 0.037λ

first voltage minimum = 0.287λ

Maxima and Minima

Practice: Solution

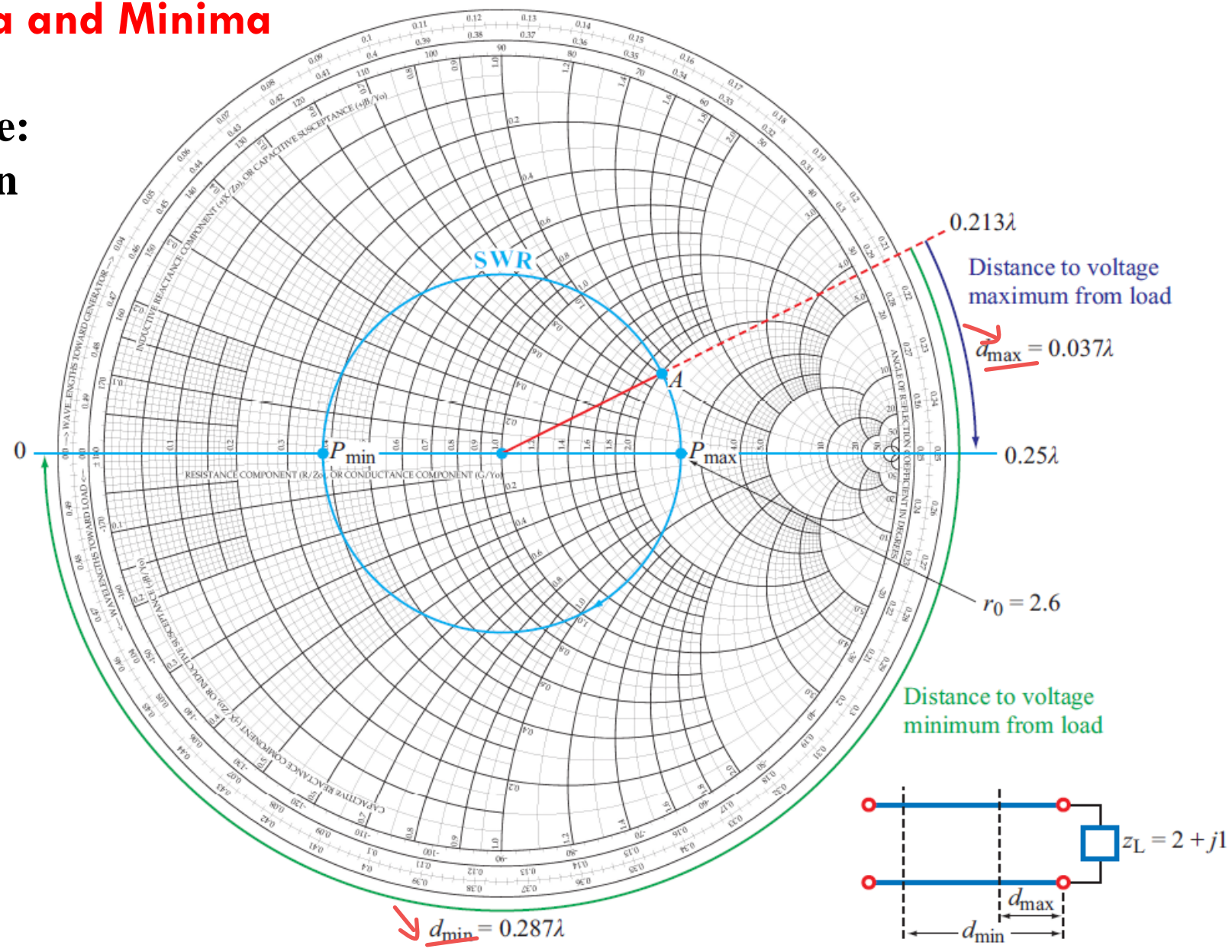



Figure 2-28: Point A represents a normalized load with $z_L = 2 + j1$. The standing wave ratio is $S = 2.6$ (at P_{max}), the distance between the load and the first voltage maximum is $d_{max} = (0.25 - 0.213)\lambda = 0.037\lambda$, and the distance between the load and the first voltage minimum is $d_{min} = (0.037 + 0.25)\lambda = 0.287\lambda$.

Practice:

A $50\text{-}\Omega$ lossless line is terminated in a load $Z_L = (25 + j50)\Omega$.

Use the smith chart to find

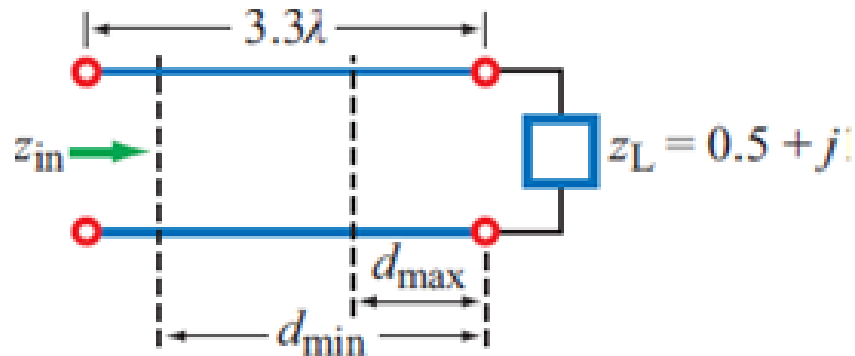- voltage reflection coefficient,
- the voltage standing-wave ratio,
- the distances of the first voltage maximum and first voltage minimum from the load,
- the input impedance of the line, given the line is 3.3λ




Practice:

A $50\text{-}\Omega$ lossless line is terminated in a load $Z_L = (25+j50)\Omega$.

Use the smith chart to find

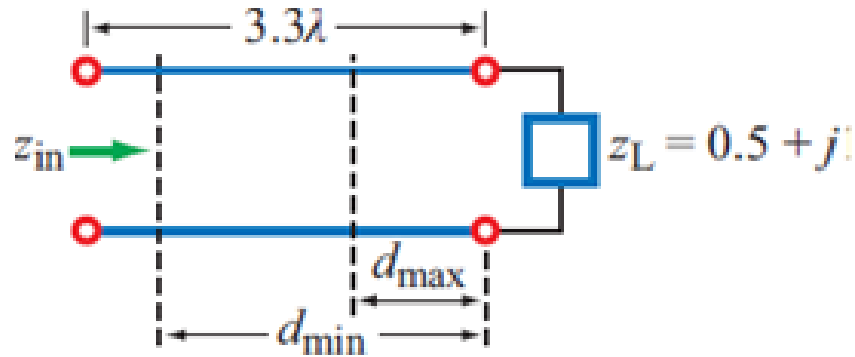- voltage reflection coefficient,
- the voltage standing-wave ratio,
- the distances of the first voltage maximum and first voltage minimum from the load,
- the input impedance of the line, given the line is 3.3λ



Ans: $Z_L = 0.5 + j1$

a) $\Gamma = 0.62 \angle 83^\circ$

b) $VSWR = 4.26$

c) $d_{max} = 0.115 \lambda$, $d_{min} = 0.365 \lambda$

d) Normalized $Z_{in} = 0.28 + j0.40$; $Z_{in} = (14-j20)\Omega$

Practice: Solution

A $50\text{-}\Omega$ lossless transmission line of length 3.3λ is terminated by a load impedance $Z_L = (25 + j50)\text{ }\Omega$. Use the Smith

$$z_L = \frac{Z_L}{Z_0} = \frac{25 + j50}{50} = 0.5 + j1$$

(a)


$$d_{\max} = (0.25 - 0.135)\lambda = 0.115\lambda$$

$$d_{\min} = (0.5 - 0.135)\lambda = 0.365\lambda$$

(b)

$$z_{\text{in}} = 0.28 - j0.40$$

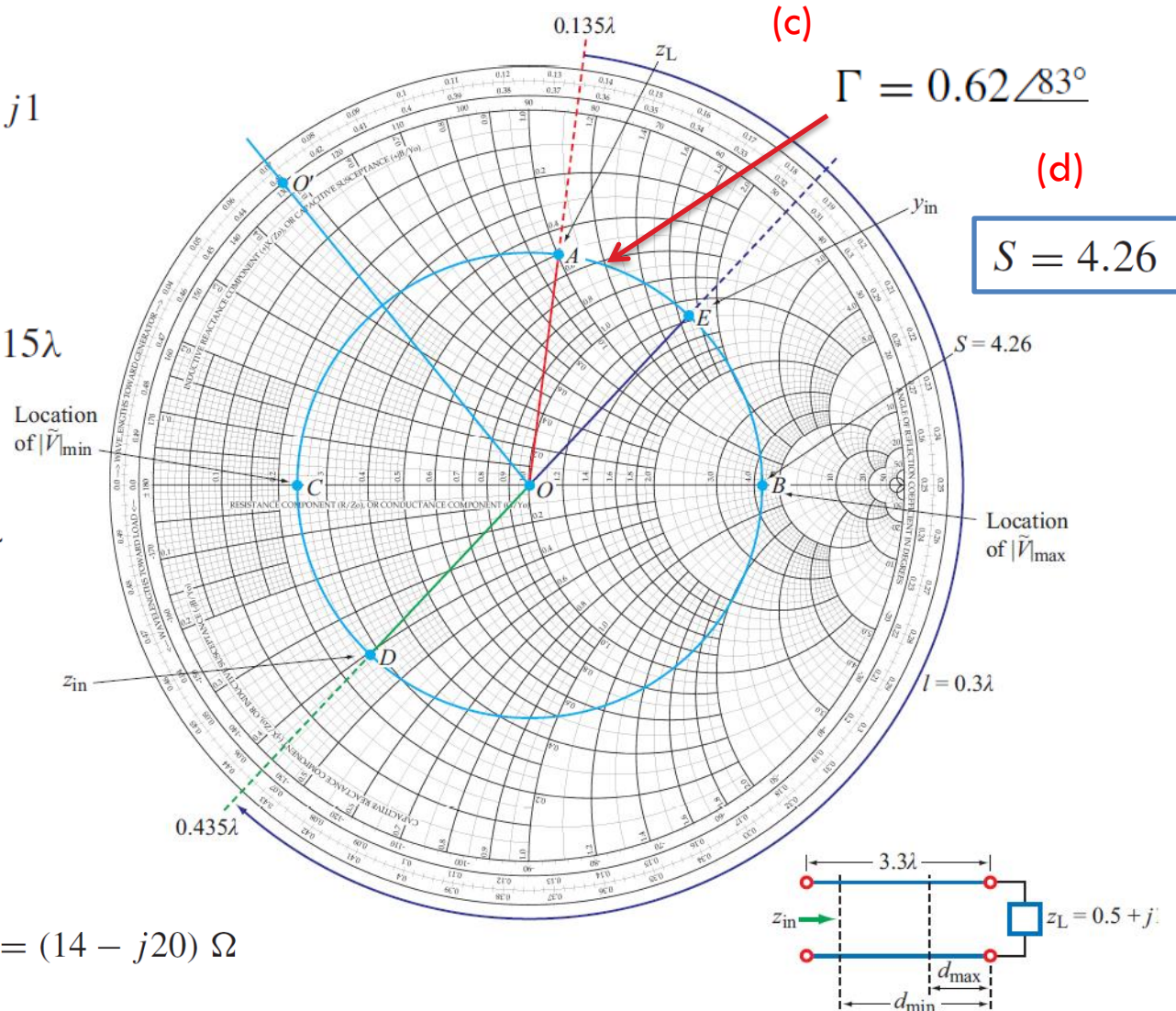
$$Z_{\text{in}} = z_{\text{in}} Z_0 = (0.28 - j0.40)50 = (14 - j20)\text{ }\Omega$$



Smith Chart slotted line example:

Given:

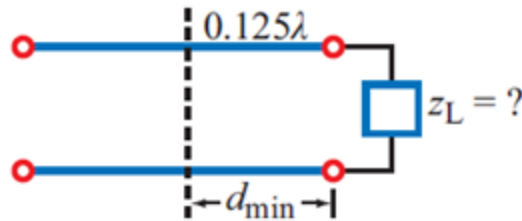$Z_0 = 50 \Omega$, $SWR = 3$, first voltage min, d_{min} is 5 cm from load and distance between adjacent minima, $\frac{\lambda}{2} = 20$ cm. Find load impedance Z_L




Solution:

Find d_{min} in wavelength format. $d_{min} = \frac{d_{min} \text{ value in cm}}{\lambda \text{ value in cm}} = \frac{5 \text{ cm}}{40 \text{ cm}} = 0.125 \lambda$

Smith Chart slotted line example.

Given:

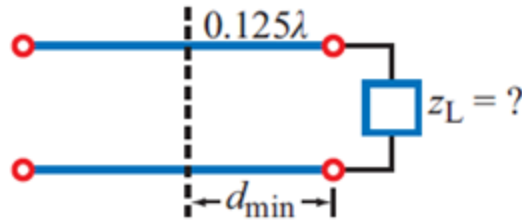$Z_0 = 50 \Omega$, $SWR = 3$, first voltage min, d_{min} is 5 cm from load and distance between adjacent minima, $\frac{\lambda}{2} = 20$ cm. Find load impedance Z_L



Solution:

Find d_{min} in wavelength format. $d_{min} = \frac{d_{min} \text{ value in cm}}{\lambda \text{ value in cm}} = \frac{5 \text{ cm}}{40 \text{ cm}} = 0.125 \lambda$

If λ is given in 0.6m then it should be converted into cm, so $\lambda = 60$ cm

$$d_{min} = \frac{d_{min} \text{ value in cm}}{\lambda \text{ value in cm}} = \frac{14.2 \text{ cm}}{40 \text{ cm}} = 0.355 \lambda$$


$$d_{min} = \frac{d_{min} \text{ value in cm}}{\lambda \text{ value in cm}} = \frac{12 \text{ cm}}{60 \text{ cm}} = 0.2 \lambda$$

Smith Chart slotted line example.

$$d_{\min} = \frac{5}{40} = 0.125\lambda$$

$$Z_L = 0.6 - j0.8$$
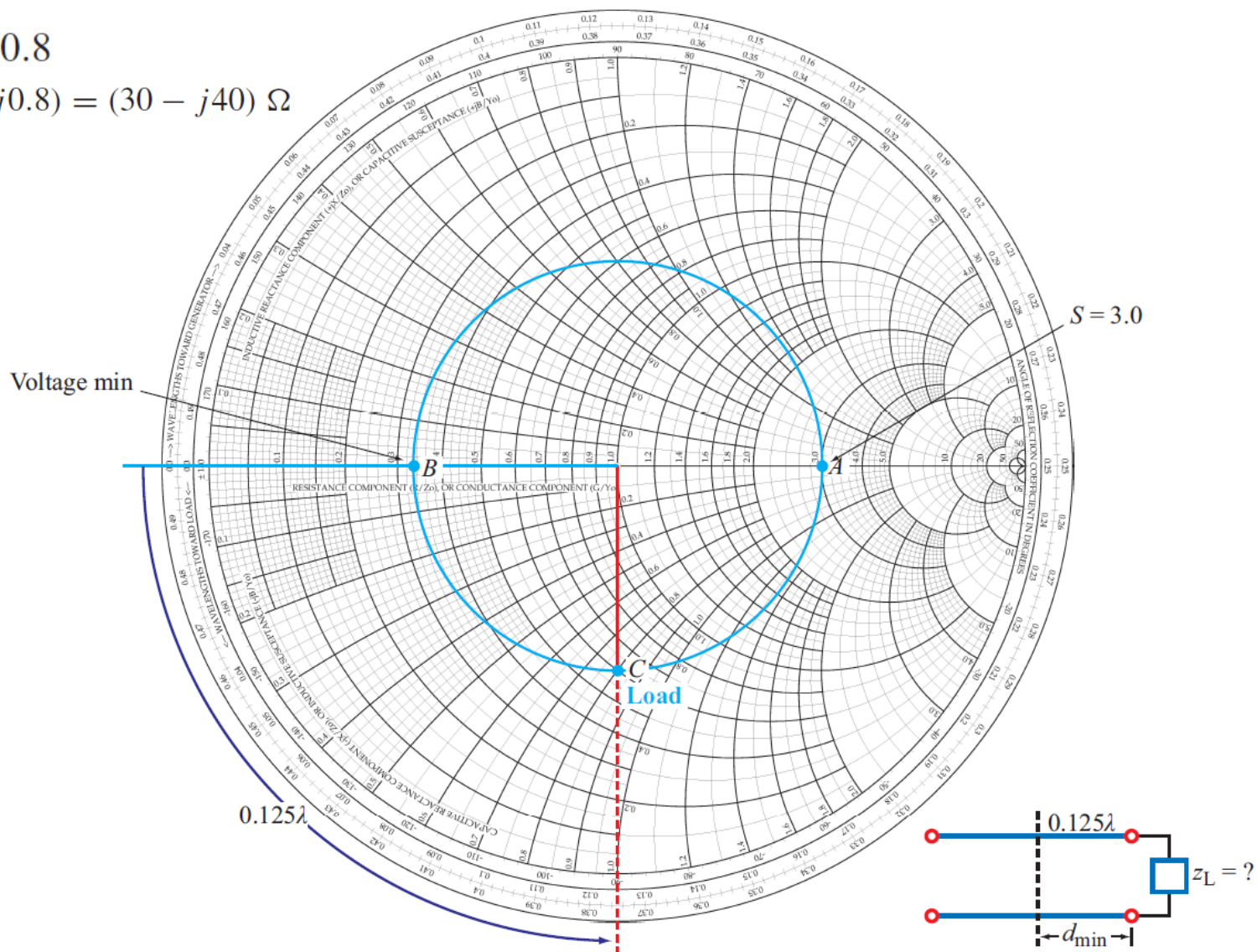
$$Z_L = 50(0.6 - j0.8) = (30 - j40) \Omega$$



Determination of Unknown
Load Impedance from
Standing Wave Data

Given $Z_0 = 50 \Omega$


$$SWR = 3.0$$

$$\lambda/2 = 20 \text{ cm}$$

$$d_{\min} = 14.2 \text{ cm} = 0.355 \lambda$$

Find \bar{Z}_R .

4.2-10

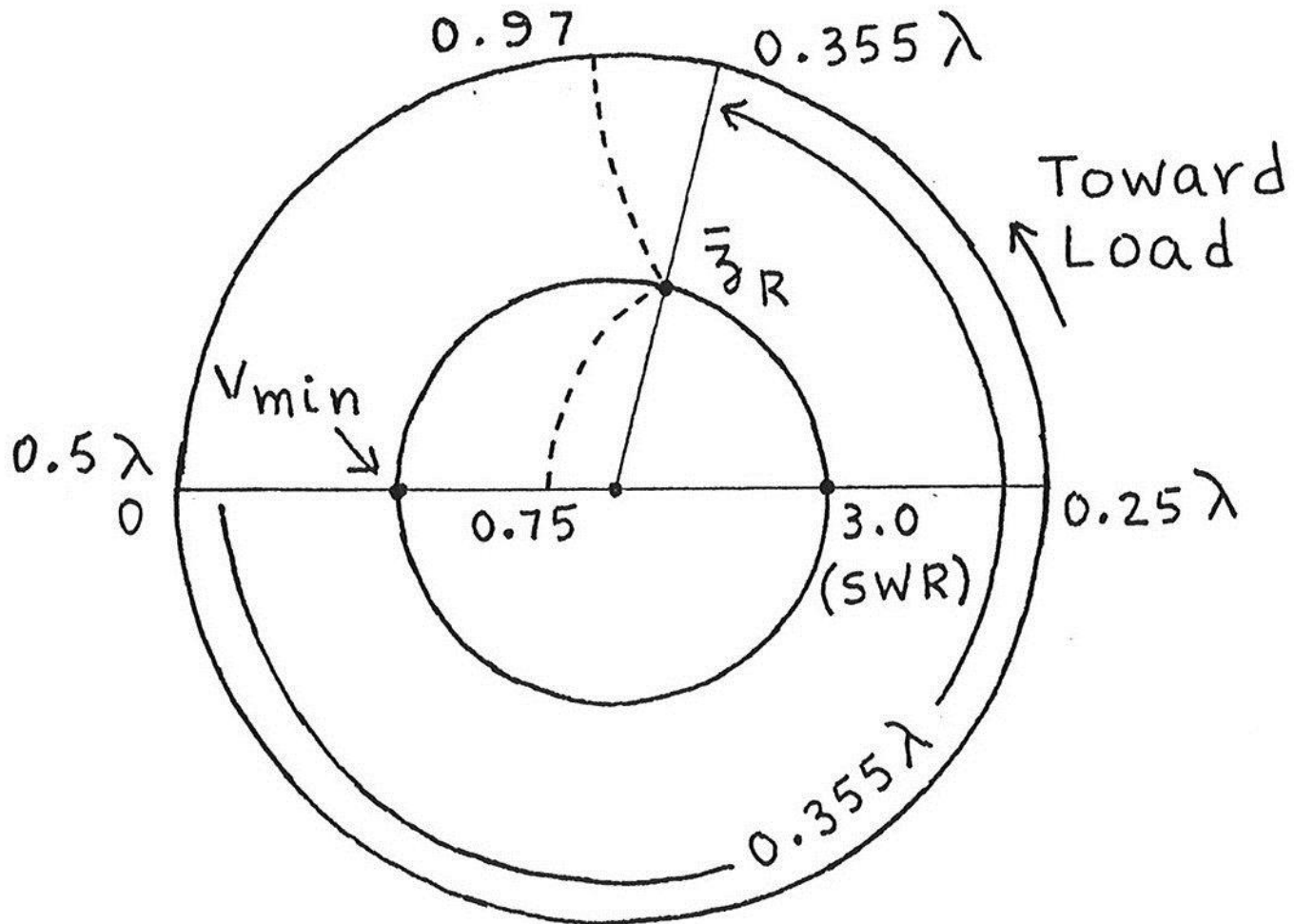

$$\bar{Z}_R = 50(0.75 + j0.97) = (37.5 + j48.5) \Omega$$